



Lab. Practice 4 (Extra part)

Optimized sequential 4x4-bit multiplier



Objective


- To reduce the number of iterations needed to calculate the multiplication based on additions.
 - Both operands will be compared and the one with lowest length will be used as index to determine the number of iterations.
 - 1. If b is the operand with the lowest length, no changes are needed.
 - 2. If a is the operand with the lowest length, registers a and b need to switch their contents.
 - If case 2 happened, an additional LED (*Switched*) will be activated.

ASM diagram

■ ASM multiplier:

```
a  = a_in;
b  = b_in;
n  = 4;
acc = 0;
Switched = 0;
if (length(a) < length(b)){
    a ⇔ b;  // atomically
    Switched = 1;
}
n = MIN(length(a), length(b));
while( n > 0 ){
    if( b(0) == 1 )
        acc = acc + a;
    a << 1;
    b >> 1;
    n --;
}
```


Modifications to be
done from here

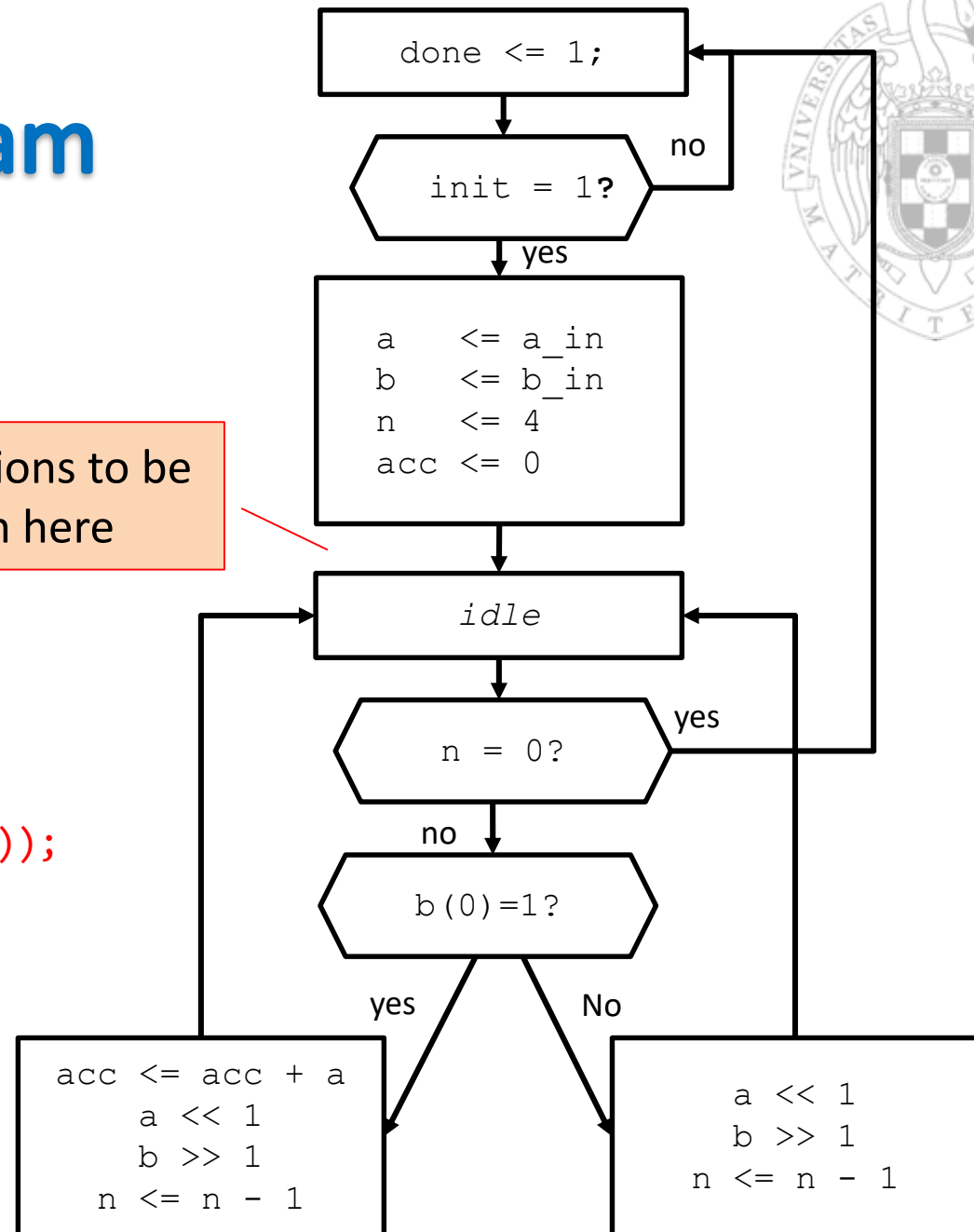



Modifications in datapath

- Two combinatorial modules at the output of numbers a and b to know the effective length of the operands. For instance:
 - a = “0110” → length = 3 bits
 - b = “1011” → length = 4 bits
- A comparator to check if $\text{length}(a) < \text{length}(b)$.
- You can also do this with 1 module whose inputs are a and b, and whose output (1 bit) compares the length of both.
- A combinatorial module that calculates the minimum of 2 numbers (a and b).
- To multiplex inputs of registers a and b to make possible the switching of values ($a \leftrightarrow b$).
- A flip-flop whose output is connected to the “*Switched*” LED.

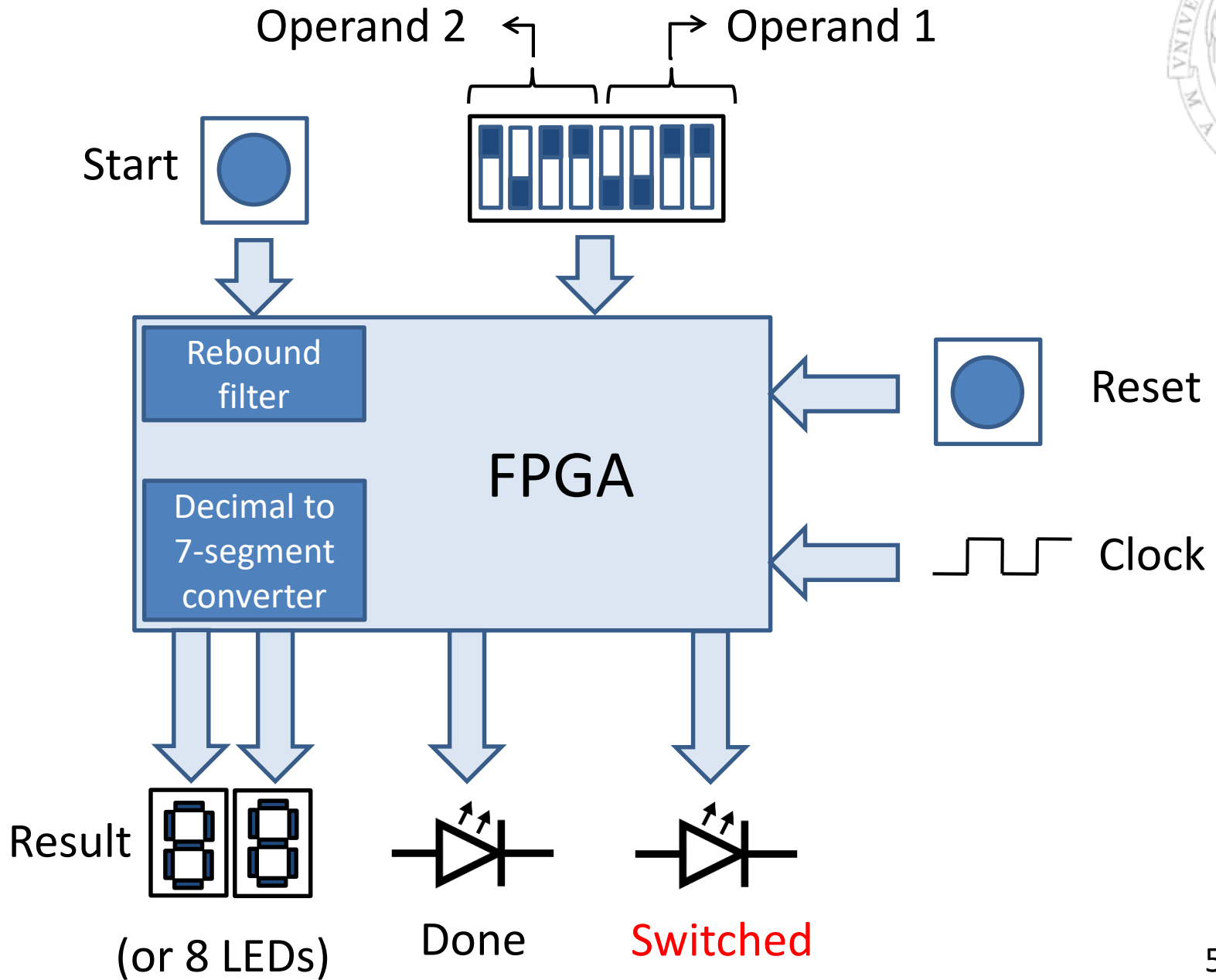

Flip-flop for *Switched*

