

Laboratory practice 6 (FINAL LAB)


MIPS multicycle



MIPS Instruction set




Instruction Formats

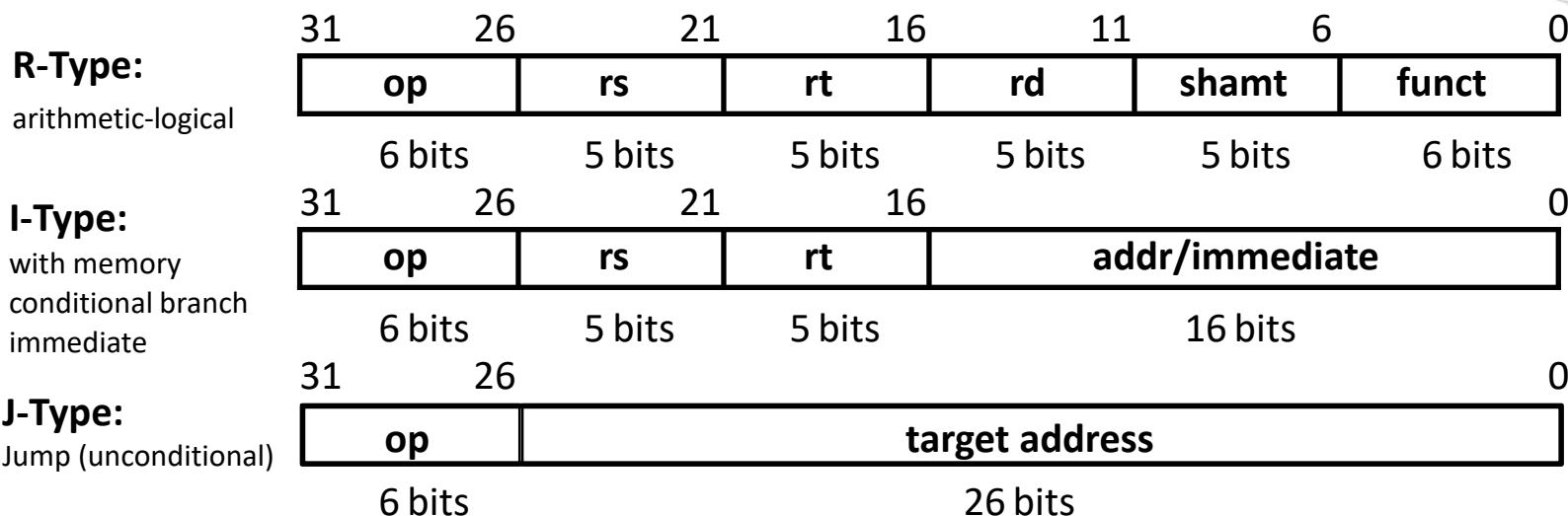

The meaning of the fields is:

- **op**: opcode
- **rs, rt, rd**: first source register, second source registers and destination register
- **shamt**: shift amount indication (shift instructions)
- **funct**: arithmetic operation
- **immediate**: branch or address displacement
- **target address**: jump target address

Multicycle Data Path design

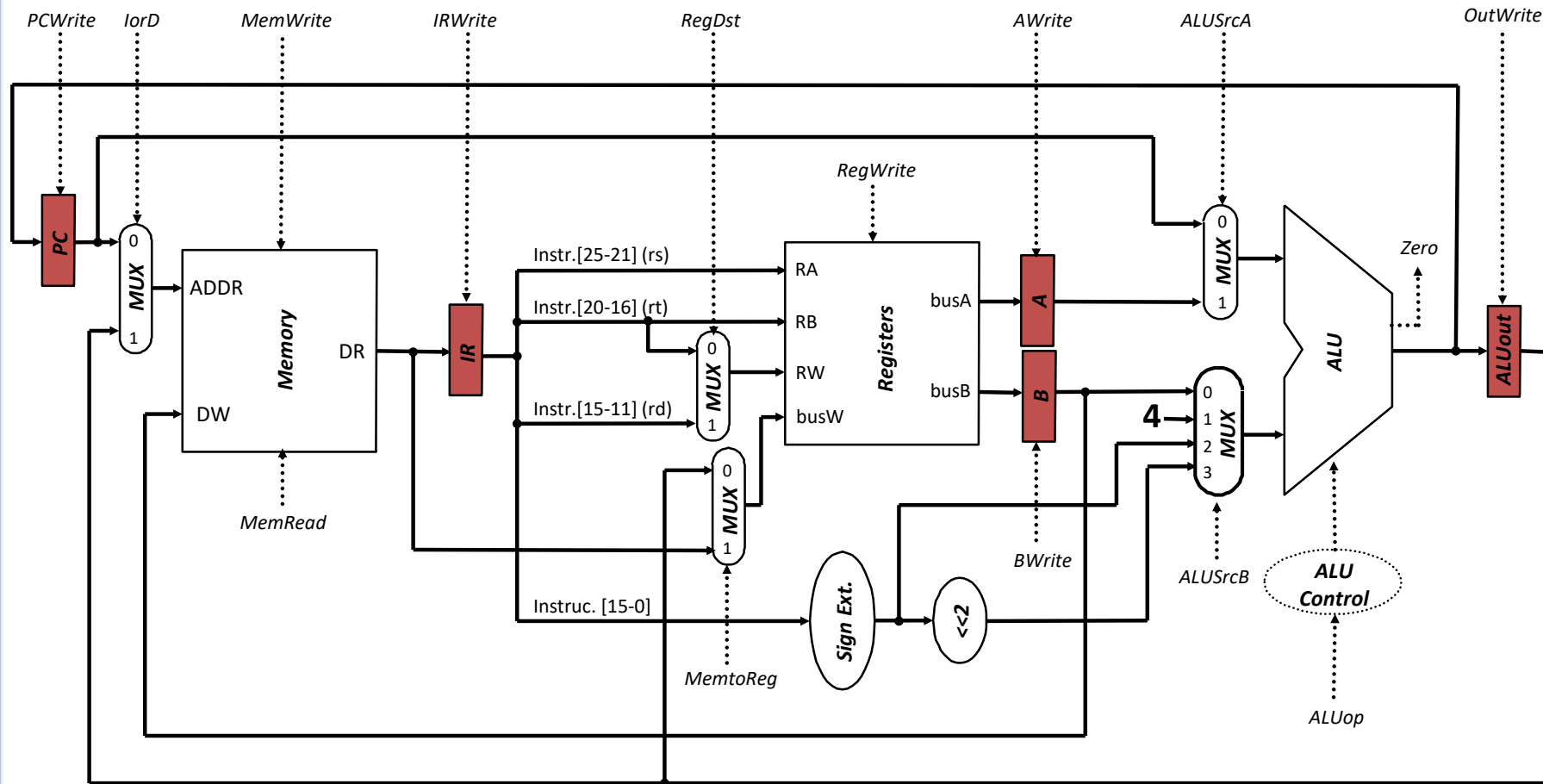

Reduced MIPS Instruction set



■ Memory instructions (load & store):

- `lw rt, immed(rs) :` `[rt<-Mem(rs+SignExt(immed)) ; PC<-PC+4]`
- `sw rt, immed(rs) :` `[Mem(rs+ SignExt(inmed))<-rt; PC<-PC+4]`


■ Arithmetic-logical:

- `add rd, rs, rt:` `[rd <- rs + rt ; PC <- PC + 4]`
- `sub rd, rs, rt:` `[rd <- rs - rt ; PC <- PC + 4]`
- `and rd, rs, rt:` `[rd <- rs and rt ; PC <- PC + 4]`
- `or rd, rs, rt:` `[rd <- rs or rt ; PC <- PC + 4]`
- `nor rd, rs, rt:` `[rd <- rs nor rt ; PC <- PC + 4]`
- `xor rd, rs, rt:` `[rd <- rs xor rt ; PC <- PC + 4]`

■ Jump (conditional):

- `beq rs, rt, inmed:`
 - `if(rs = rt) then` `PC <- PC + 4 + 4*SignExt(immed)`
 - `else` `PC <- PC + 4`

Multicycle Control Unit design

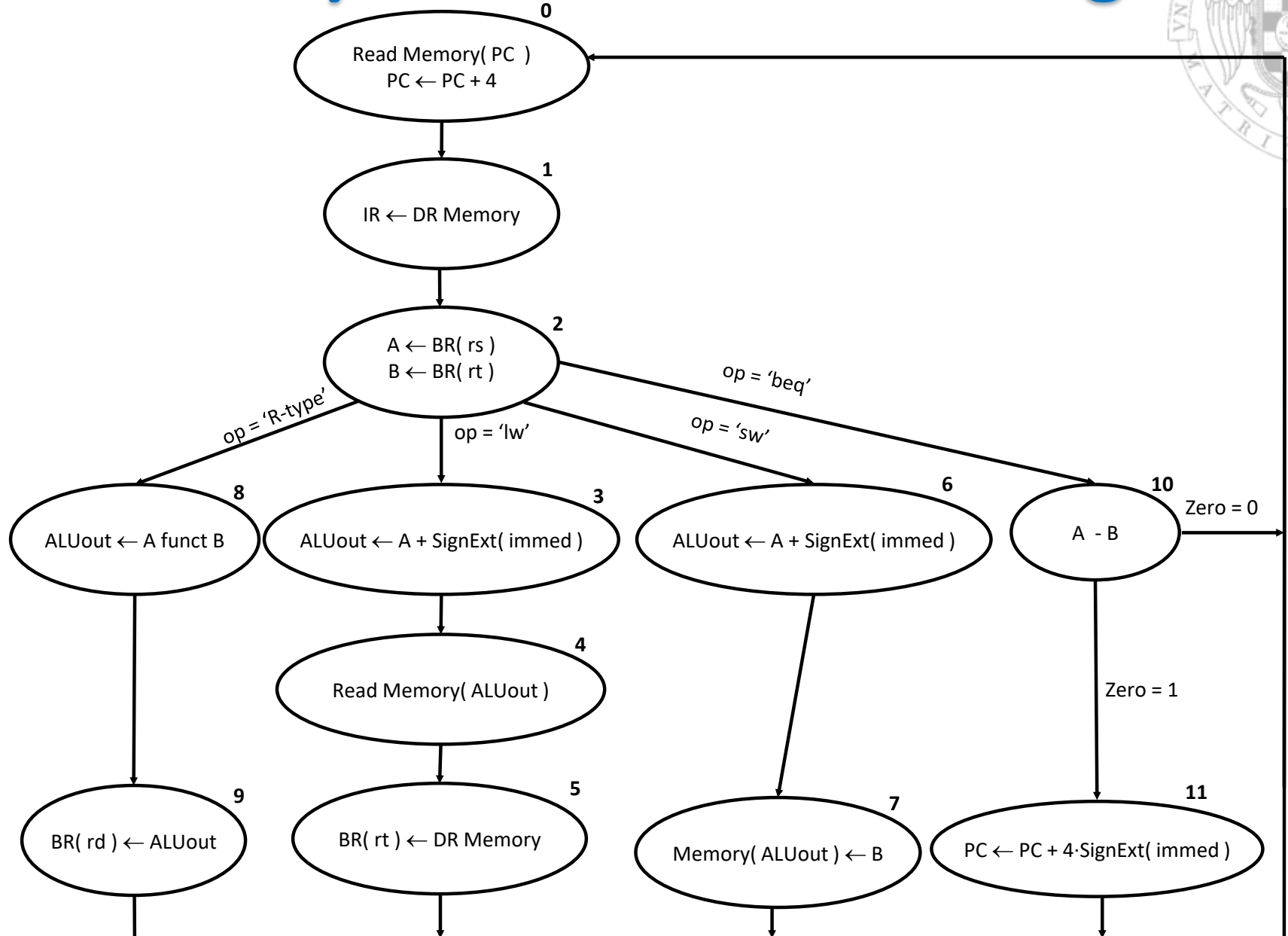

Multicycle Control Unit design



Current State	op	Zero	Next State	IRWrite	PCWrite	AWrite	BWrite	ALUSrcA	ALUSrcB	ALUOp	OutWrite	MemWrite	MemRead	lorD	MDRWrite	MemtoReg	RegDest	RegWrite
0000	XXXXXX	X	0001	0	1			0	01	00 (add)		0	1	0				0
0001	XXXXXX	X	0010	1	0							0	0	0				0
0010	100011 (lw)	X	0011	0	0	1	1					0	0					0
0010	101011 (sw)	X	0110															
0010	000000 (R-Type)	X	1000															
0010	000100 (beq)	X	1010															
0011	XXXXXX	X	0100	0	0			1	10	00 (add)	1	0	0					0
0100	XXXXXX	X	0101	0	0							0	1	1	1			0
0101	XXXXXX	X	0000	0	0							0	0			1	0	1
0110	XXXXXX	X	0111	0	0		0	1	10	00 (add)	1	0	0					0
0111	XXXXXX	X	0000	0	0							1	0	1				0
1000	XXXXXX	X	1001	0	0			1	00	10 (funct)	1	0	0					0
1001	XXXXXX	X	0000	0	0							0	0			0	1	1
1010	XXXXXX	0	0000	0	0			1	00	01 (sub)		0	0					0
1010	XXXXXX	1	1011															
1011	XXXXXX	X	0000	0	1			0	11	00 (add)		0	0					0

Homework



- Include three new instructions:
 - **Move** with register
 - **Move** with immediate
 - **Jump** unconditional
- Test these instructions in the simulator:
 - Modify the `BlockRam` code to include the new instructions.
 - **Configure and save wave configuration**
 - Inspect RAM memory, PC, IR, register bank, etc.




Move instructions

■ Move instruction with immediate:

– `mv rt, #immed` : $[rt \leftarrow \text{SignExt}(\text{immed}); PC \leftarrow PC + 4]$

I-Type:

with memory
conditional branch
immediate

 


- Opcode: "010000"

■ Move with register:

– `mv rt, rs` : $[rt \leftarrow rs ; PC \leftarrow PC + 4]$

I-Type:

with memory
conditional branch
immediate

 

- Opcode: "010010"



Move instructions

- Modify the **BlockRam** program using the move instruction to set the registers to 0 and 1

1. **R3** register will be initialized to 0 like this:

- `mv r3, #0`

Opcode	rt	Immediate	
010000	00000	00011	00000000000000000000 -> x"40030000"

2. Register **R4** will be initialized to 0 by copying the **R3** register like this:

- `mv r4, r3`

3. **R2** register will be initialized to 1 like this:


- `mv r2, #1`



Jump unconditional

■ Jump instruction :

 – `j addr` : $PC \leftarrow 0000 \ \& \ \text{addr} \ \& \ 00$



- Opcode: “000010”

■ Modify the **BlockRam** program using the jump instruction to replace:

– `beq R0, R0, ADDR` -> `j ADDR`



Grading

- Previous work is just to familiarize yourself with the processor.
 - Upload the vhd files at the beginning of the session.
- During the exam you must implement two new instructions (1.25pts each)
- The laboratory exam is **NOT** recoverable